


Hardware Fundamentals [CESE4005]

Lecture 1.1: Introduction to FET transistors,
CMOS gates and semiconductors

September 2024

Transistor: The Building Block of Computers

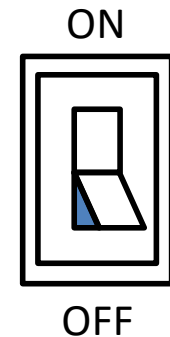- Microprocessors contain billions of transistors
 - Intel Broadwell-E5 (2016): 7 billion
 - IBM Power 9 (2017): 8 billion
 - Intel Ponte Vecchio (2021): 100 billion (is it a CPU?)
- Logically, each transistor acts as a **switch**
- Combined to implement **logic functions**
 - AND, OR, NOT, ...




Combined to build **higher-level structures**

- Adder, multiplexer, decoder, register, ...

Combined to build a **processor**

- RISC-V (but also LC-3)

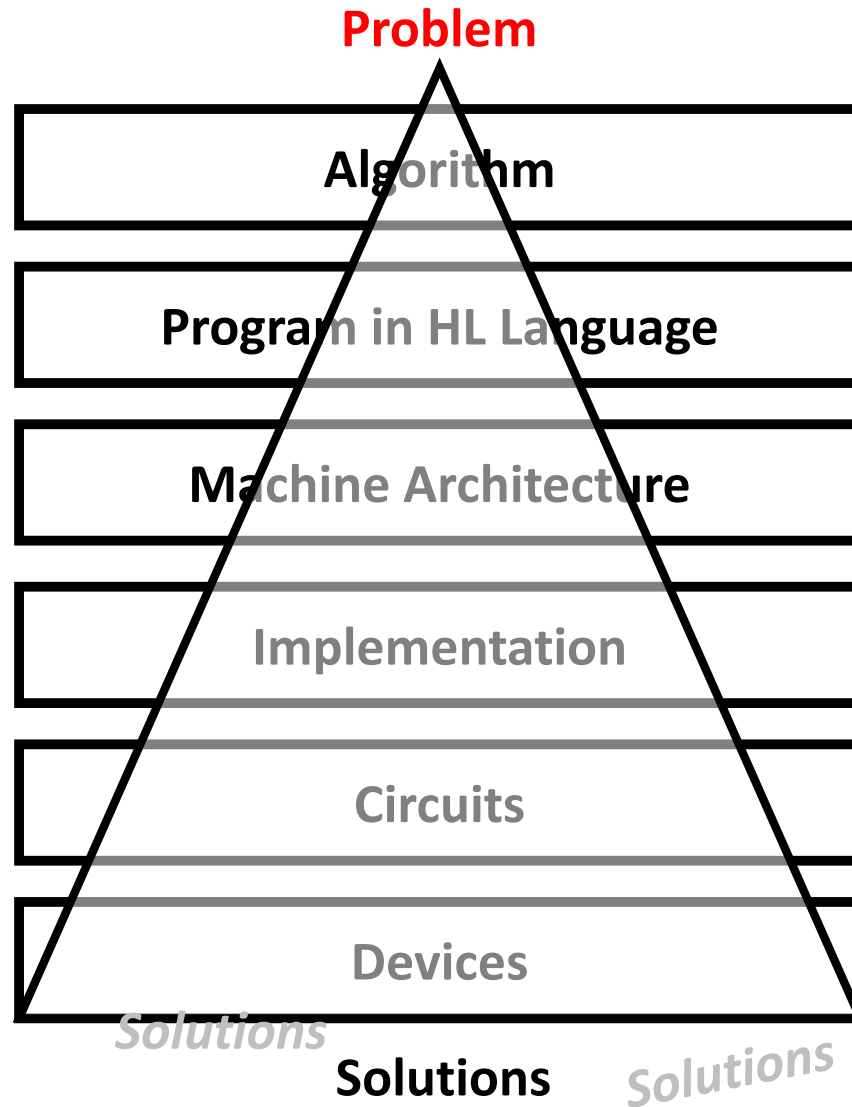Transistors position in the computing stack



(by moving electrons)

Moore's Law: The number of transistors on microchips doubles every two years. Our World in Data

Moore's law describes the empirical regularity that the number of transistors on integrated circuits doubles approximately every two years. This advancement is important for other aspects of technological progress in computing – such as processing speed or the price of computers.

Transistor count

50,000,000,000

10,000,000,000

5,000,000,000

1,000,000,000

500,000,000

100,000,000

50,000,000

10,000,000

5,000,000

1,000,000

500,000

100,000

50,000

10,000

5,000

1,000

Year in which the microchip was first introduced

1970

1972

1974

1976

1978

1980

1982

1984

1986

1988

1990

1992

1994

1996

1998

2000

2002

2004

2006

2008

2010

2012

2014


2016

2018


2020

Data source: Wikipedia (wikipedia.org/wiki/Transistor_count)
OurWorldinData.org – Research and data to make progress against the world's largest problems. Licensed under CC-BY by the authors Hannah Ritchie and Max Roser.

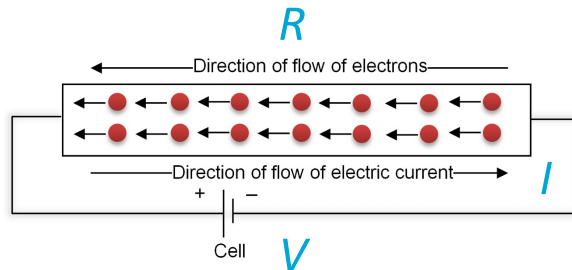Very Basic Electrical Circuits Cheat Sheet




Resistor R

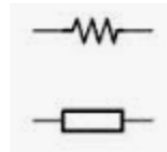

conductor

Capacitor C

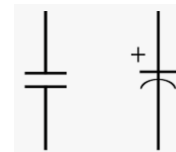

insulator

?

Ohm's Law

$$I = \frac{V_T}{R}$$

Voltage Drop

$$V_x = I_x * R_x$$

Watt's Law

$$P = V_T * I$$

Current

$$I = \frac{q}{t}$$

$$1 \text{ C} = 6.25 * 10^{18} \text{ electrons}$$

Series circuits
(sub-circuits)

$$I_T = I_1 = I_2 = I_3 = \dots$$

$$R_T = R_1 + R_2 + R_3 + \dots$$

$$I_T = \frac{V_T}{R_T}$$

KVL

$$V_T = V_1 + V_2 + V_3 + \dots$$

Voltage Division
(for series resistors)

$$V_x = \frac{R_x}{R_T} * V_T$$

Power

$$P = V_T I = I^2 R = \frac{V_T^2}{R}$$


$$1 \text{ hp} = 746 \text{ W}$$

Energy


$$\text{Energy} = P t$$

$$\text{Cost} = \text{Energy} * \frac{\text{cost}}{\text{kW}\cdot\text{h}}$$

P in kW
t in h
Energy in kW•h

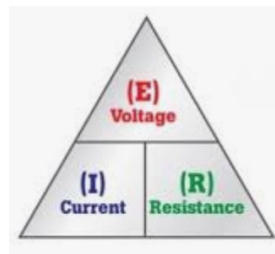

...

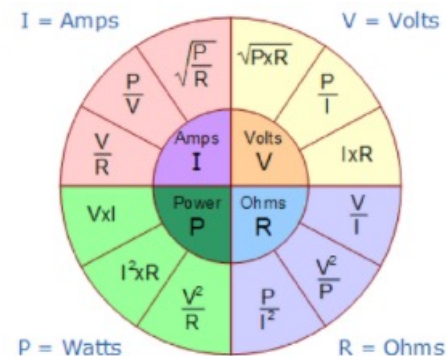

Parallel circuits
(sub-circuits)

$$V_T = V_1 = V_2 = V_3 = \dots$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

$$I_T = \frac{V_T}{R_T}$$

KCL

$$I_T = I_1 + I_2 + I_3 + \dots$$

Current Division
(for parallel resistors)

$$I_x = \frac{R_{eq}}{R_x} * I_T$$

Current Division
(for 2 parallel resistors)

$$I_x = \frac{\text{Opposite}}{\text{Sum}} * I_T$$

Two resistors in parallel

$$R_1 \parallel R_2 = \frac{R_1 * R_2}{(R_1 + R_2)}$$

n equal resistors in parallel

$$R_T = \frac{R}{n}$$


Conductance

$$G = \frac{1}{R}$$

$$G_T = G_1 + G_2 + G_3 + \dots$$

$$I_T = V_T G_T$$

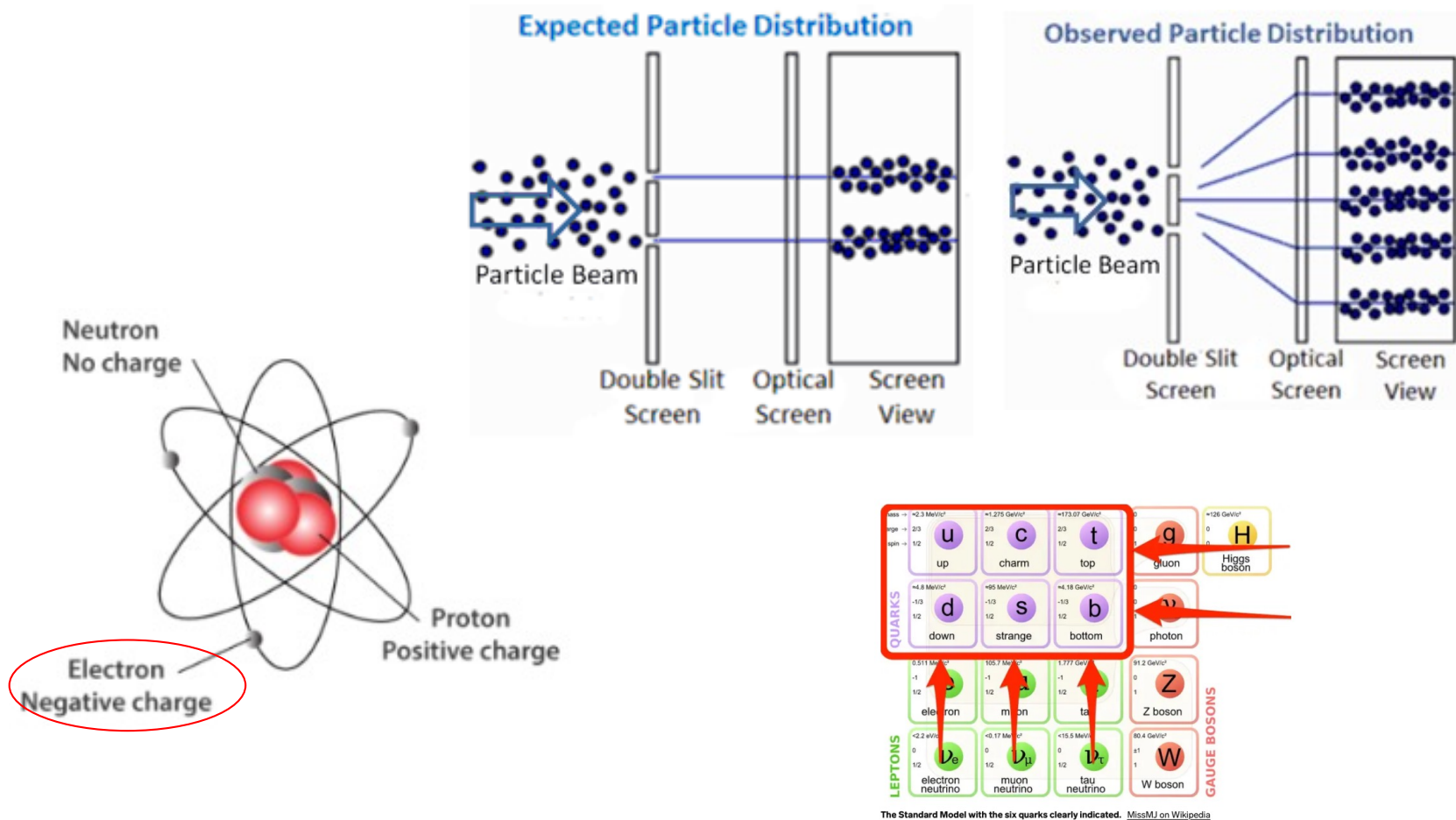
Electrons must be important particles (however)



Physicists just discovered a different type of particle that will spawn an entirely new field of research

A Simple Switch Circuit

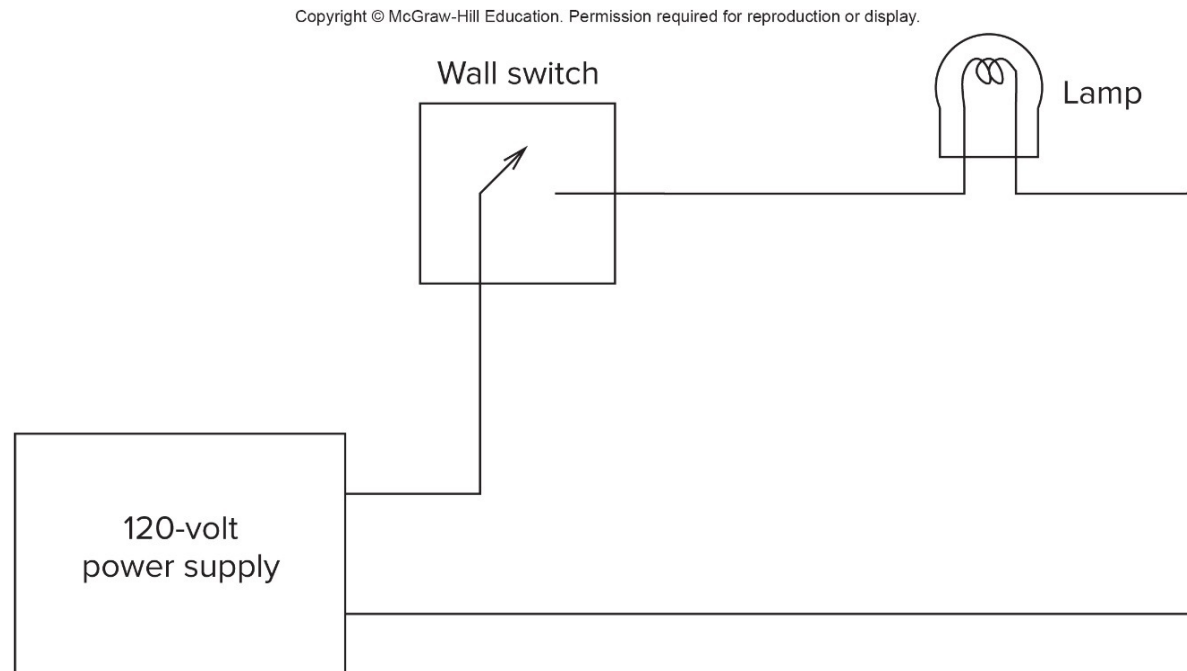- A wall switch determines whether current flows through the light bulb




- If switch is closed, current flows, lamp is **ON**, voltage across lamp is **non-zero**
- If switch is open, no current flows, lamp is **OFF**, voltage across lamp is **zero**

Transistor = Voltage-Controlled Switch 1

- Figure shows an **N-type** transistor
When Gate voltage is **positive**, relative to Source, transistor acts as a short circuit: a **closed** switch
- When Gate voltage is **zero** (or negative), relative to Source, transistor acts as an open circuit: an **open** switch

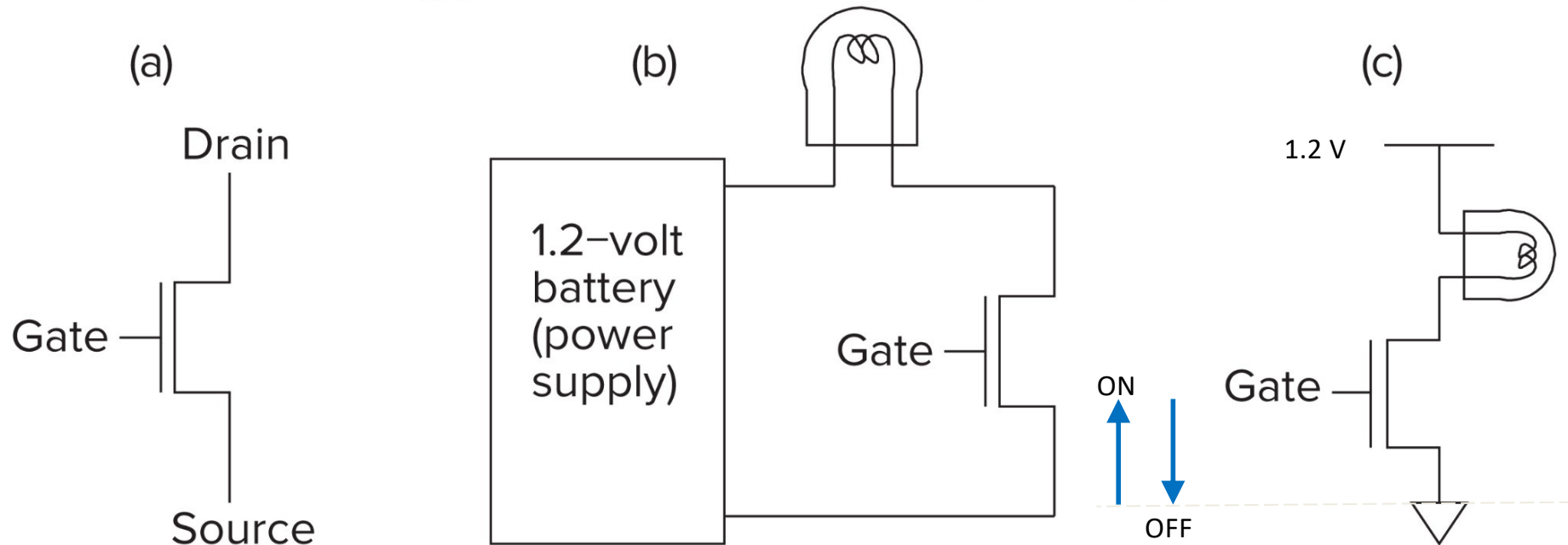
Copyright © McGraw-Hill Education. Permission required for reproduction or display.



Transistor = Voltage-Controlled Switch 2

- Consider the circuit below. The bar at the top represents the high voltage rail (+1.2V) and the triangle at the bottom represents ground (0V)

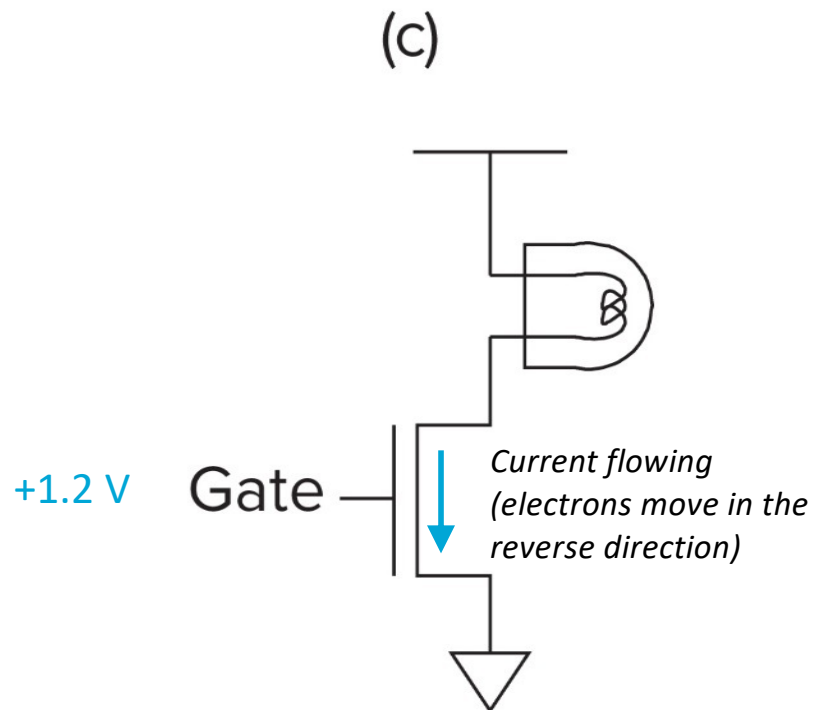Copyright © McGraw-Hill Education. Permission required for reproduction or display.



- When Gate = +1.2V, what happens?**


- Gate-to-source voltage > 0
- Transistor = closed switch
- Current flows, lamp is **ON**

- When Gate = 0V, what happens?**

- Gate-to-source voltage = 0
- Transistor = open switch
- No current flows, lamp is **OFF**

Transistor = Voltage-Controlled Switch 3

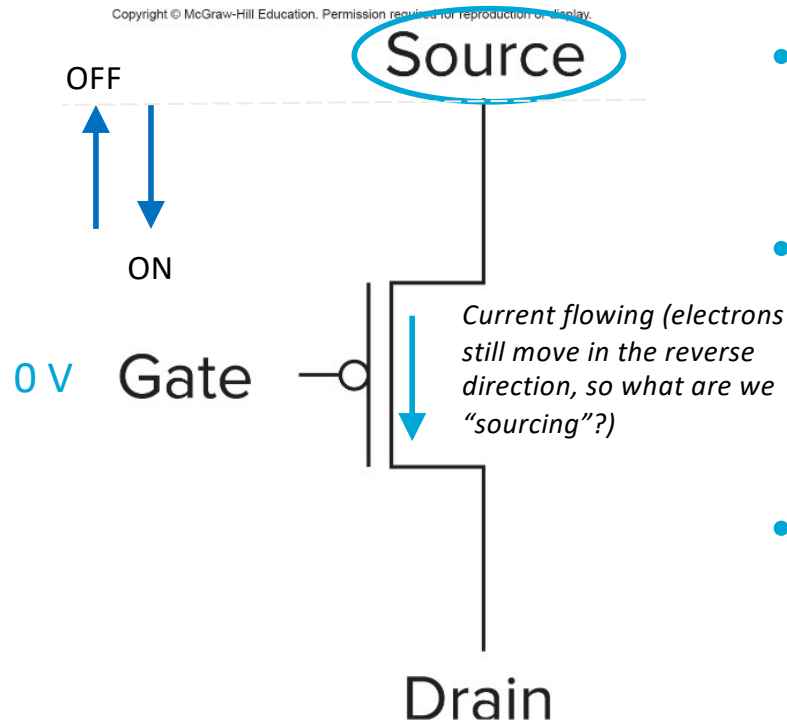- A different type of transistor is shown below, the **P-type** transistor. Notice the little "bubble" on its gate




- When Gate voltage is **negative**, relative to Source, transistor acts as a short circuit: a **closed** switch
- When Gate voltage is **zero** (or positive), relative to Source, transistor acts as an open circuit: an **open** switch
- NOTE: This behavior is the opposite of the N-type. Behavior is complementary

- We use both N-type and P-type transistors together to implement logic gates. This is known as **CMOS** or Complementary MOS logic


Logic Gate

- A logic gate is a circuit that transforms binary input signals into a single binary output signal. Signals are the voltages.
- Binary: $+1.2V = 1$ (true), $0V = 0$ (false)
 - **P-type transistors**: source connected to $+1.2V$
 - When gate = 1, transistor is OFF
 - When gate = 0, transistor is ON
 - **N-type transistors**: source connected to $0V$
 - When gate = 1, transistor is ON
 - When gate = 0, transistor is OFF

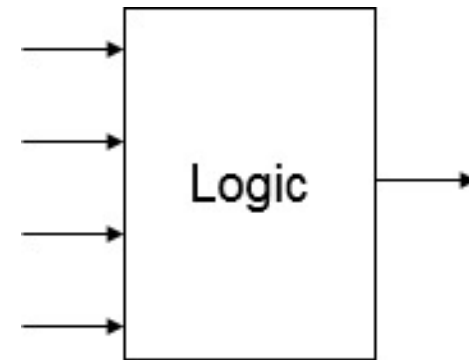

NOT Gate (Inverter)

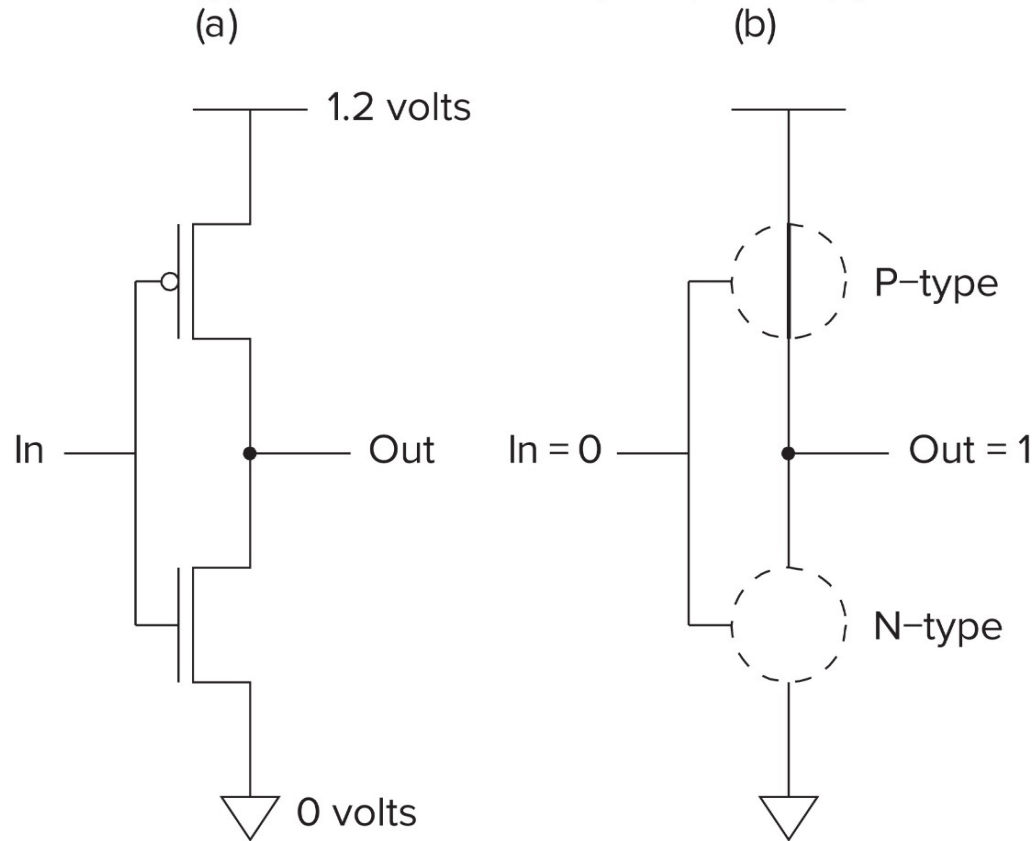Copyright © McGraw-Hill Education. Permission required for reproduction or display.





- **Example:**
- When input = 0, P-type transistor turns on and N-type transistor turns off. Output is connected to +1.2V, so output = 1
- Logic gate is described using its **truth table**

Input	Output
0	1
1	0



Inverter (animated)

A	Y
0	
1	0

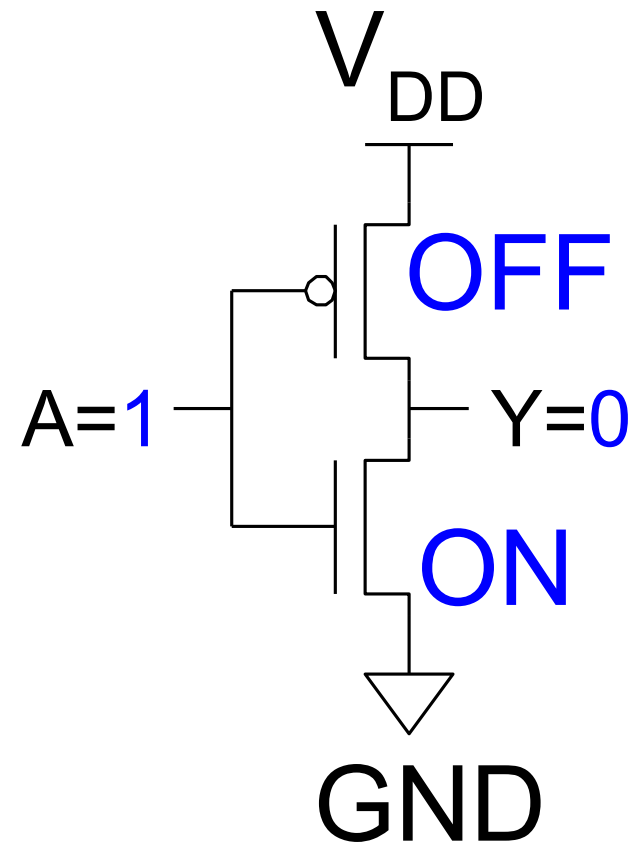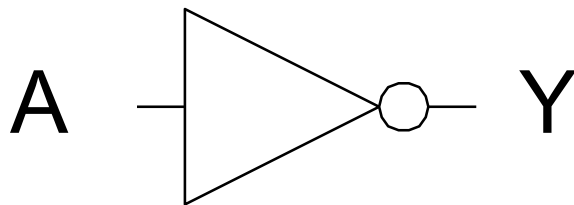

Inverter (animated)

A	Y
0	1
1	0

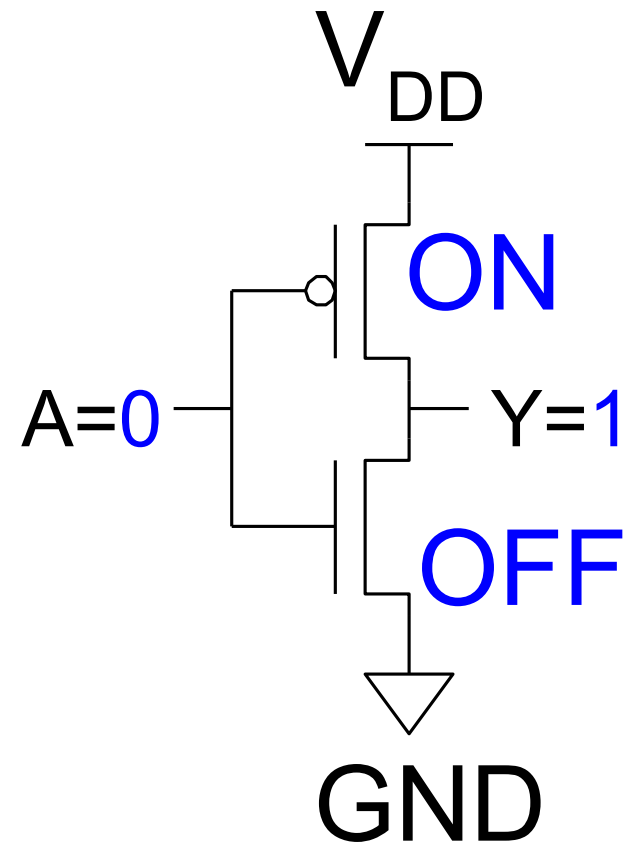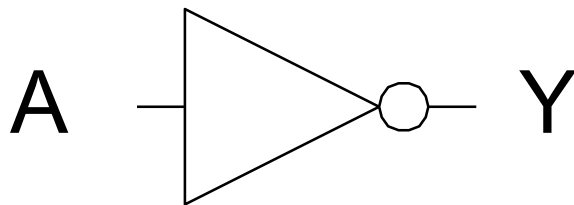


NOR Gate


- When either input is 1, output is 0

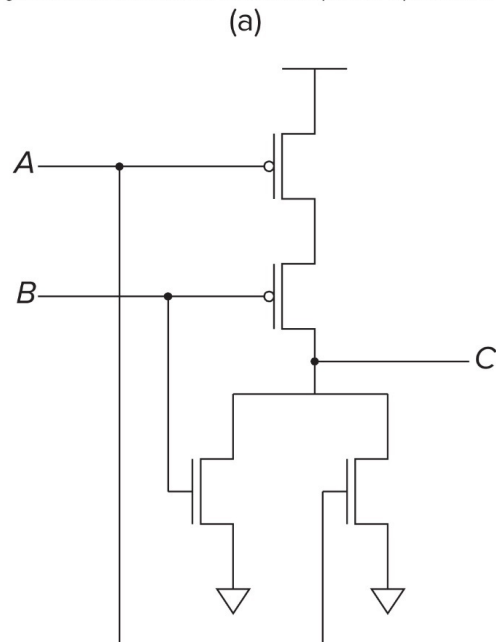- Example:**
- When $B = 1$, N-type transistor turns on and output (C) is connected to GND. Both inputs must be 0 to connect C to +1.2V.

Copyright © McGraw-Hill Education. Permission required for reproduction or display.



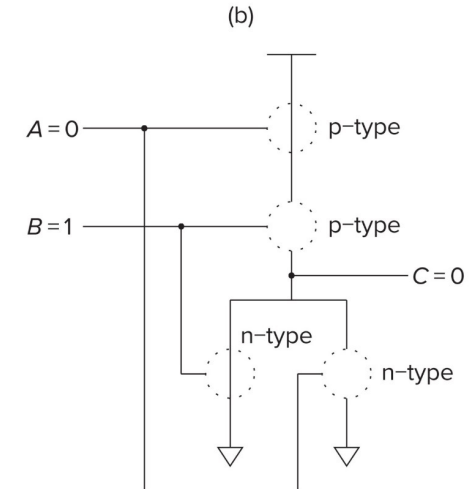Copyright © McGraw-Hill Education. Permission required for reproduction or display.




A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

$$C = \text{NOT}(A \text{ OR } B)$$


The OR Gate

- When either input is 1, output is 1
Add NOT after NOR

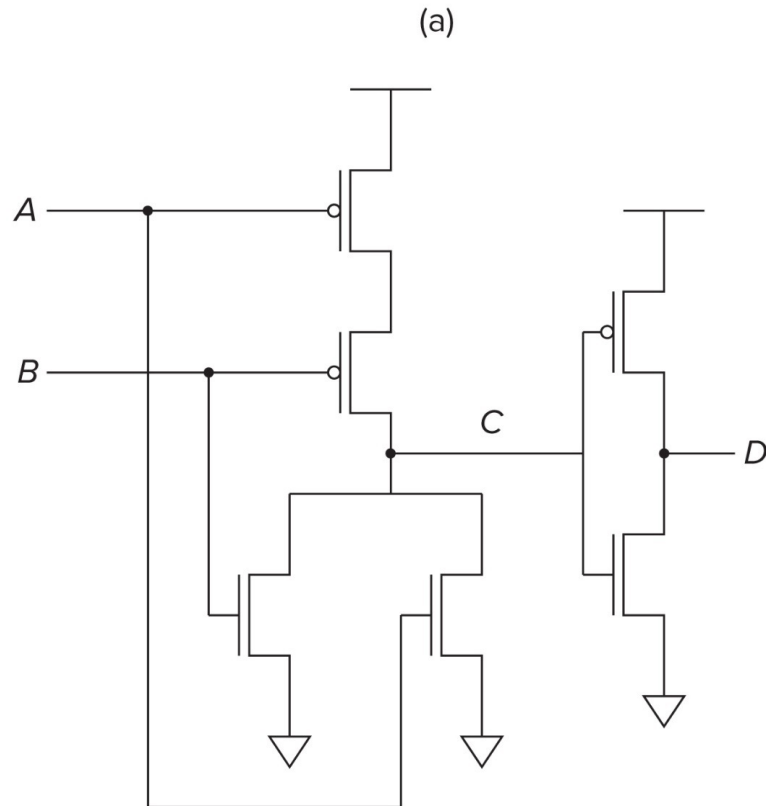Copyright © McGraw-Hill Education. Permission required for reproduction or display.



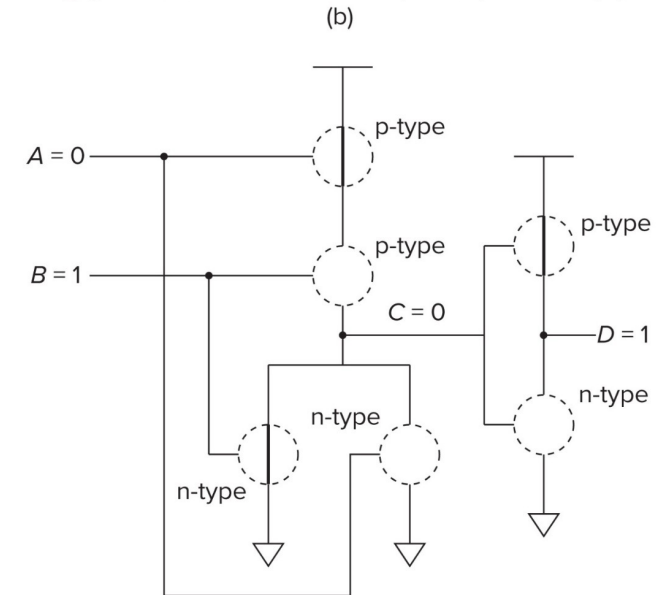Copyright © McGraw-Hill Education. Permission required for reproduction or display.




A	B	C	D
0	0	1	0
0	1	0	1
1	0	0	1
1	1	0	1

Why do we need NOT after NOR?

- Why can't we simply put the P-type on the bottom and the N-type on top?

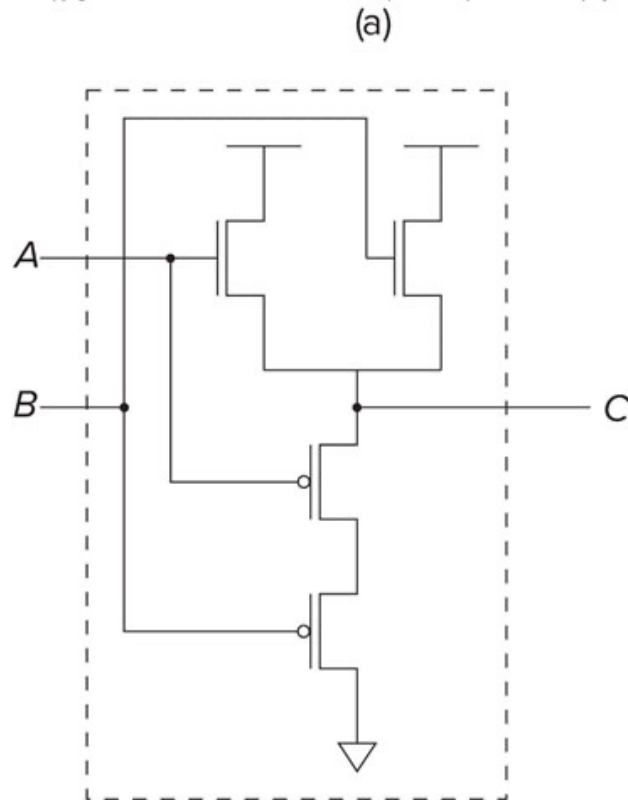Copyright © McGraw-Hill Education. Permission required for reproduction or display.



(b)




<i>A</i>	<i>B</i>	<i>C</i>
0 volts	0 volts	1.0 volts
0 volts	1.2 volts	0.7 volts
1.2 volts	0 volts	0.7 volts
1.2 volts	1.2 volts	0.7 volts

- Does not work because of the electrical properties of the transistors.*
- Must **always** connect P to + and N to GND for CMOS circuit to work properly.


Maybe we should get to know more about transistors/electrons?

Semiconductor basics

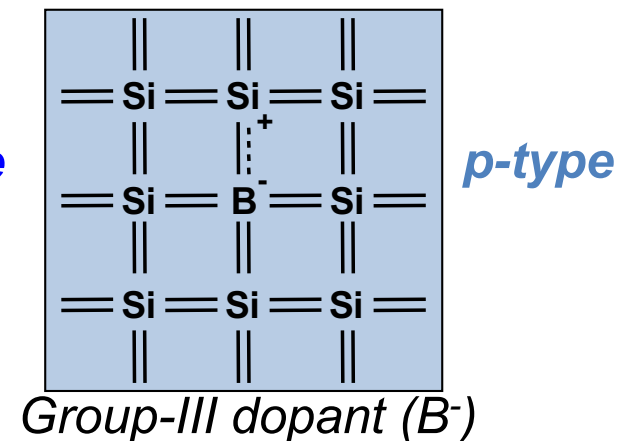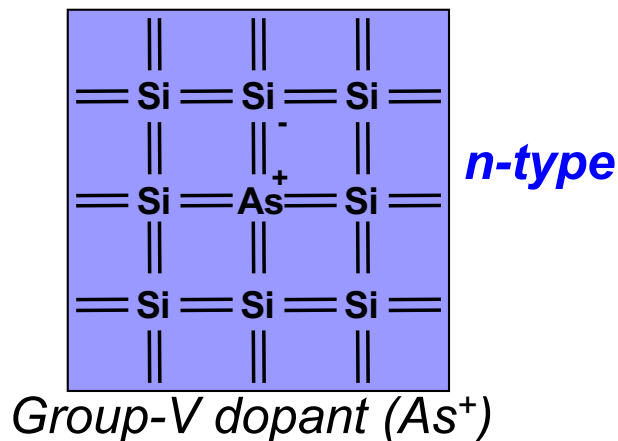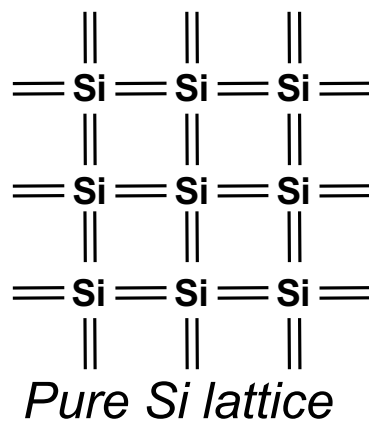
- Pure silicon (Si) is a very regular 3D-lattice (figure A)
- Conductivity is increased through *doping*, i.e. introducing impurities to this lattice (figures B and C)



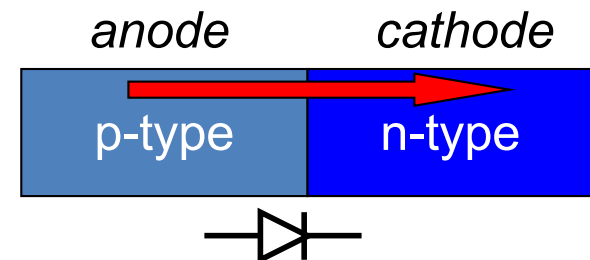
- **Extra** electrons: negative-charged, free carriers
- **Missing** electrons (“holes”): positive-charged, free carriers
- A **pn**-sandwich (“**pn**-junction”) effectively is a *diode*




Semiconductor basics (more)

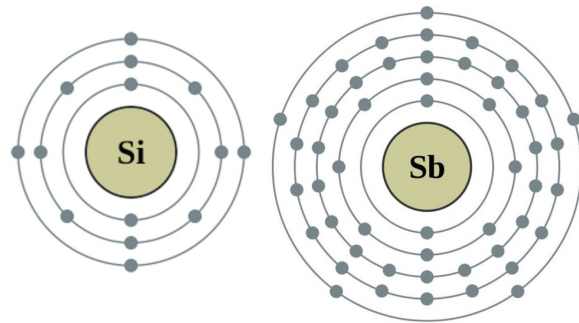


Silicon (Si) + Antimony (Sb)

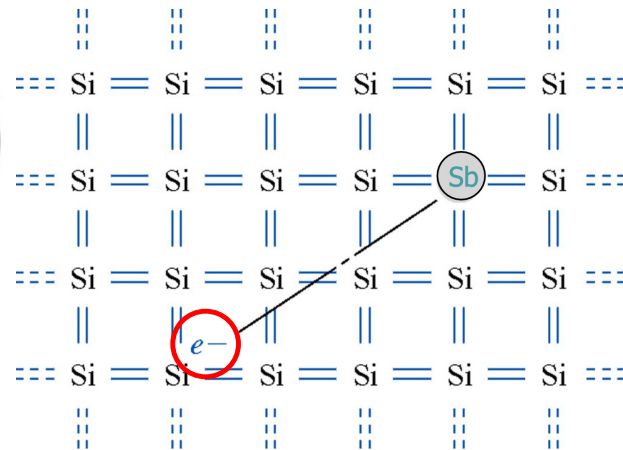

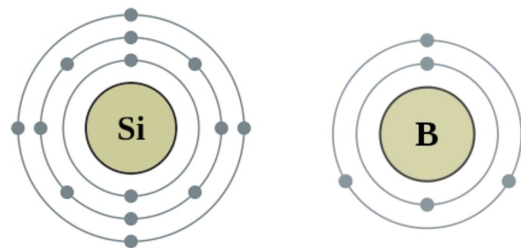The **donor** electron can become free with very small amount of thermal energy. (n-type)





Silicon (Si) + Boron (B)

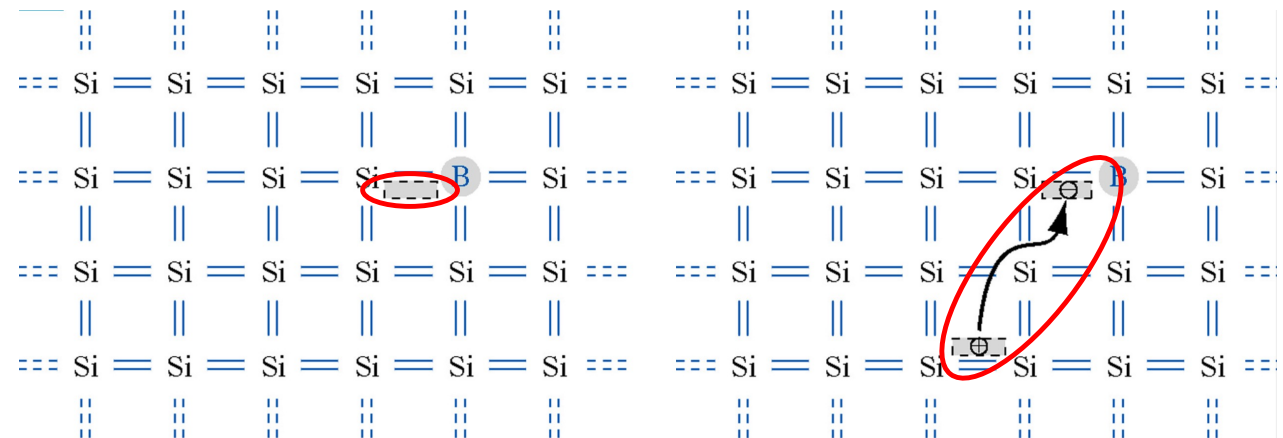

The **acceptor** has only three covalent electrons leaving one bond incomplete. With little thermal energy, valence electron breaks from a covalent bond and occupies this position (creating a hole). (p-type)

Q: which of the two conducts better?

Semiconductor basics (conductance)

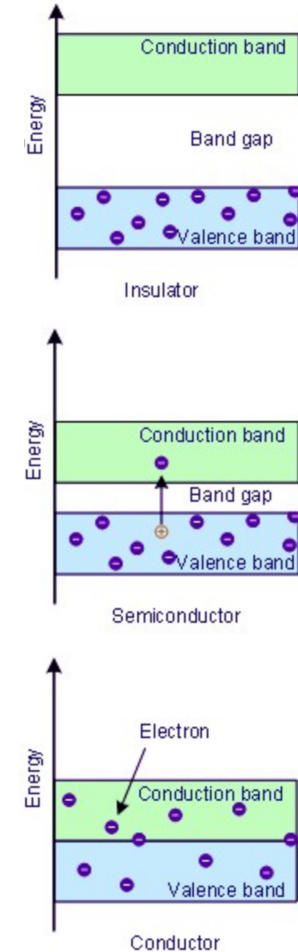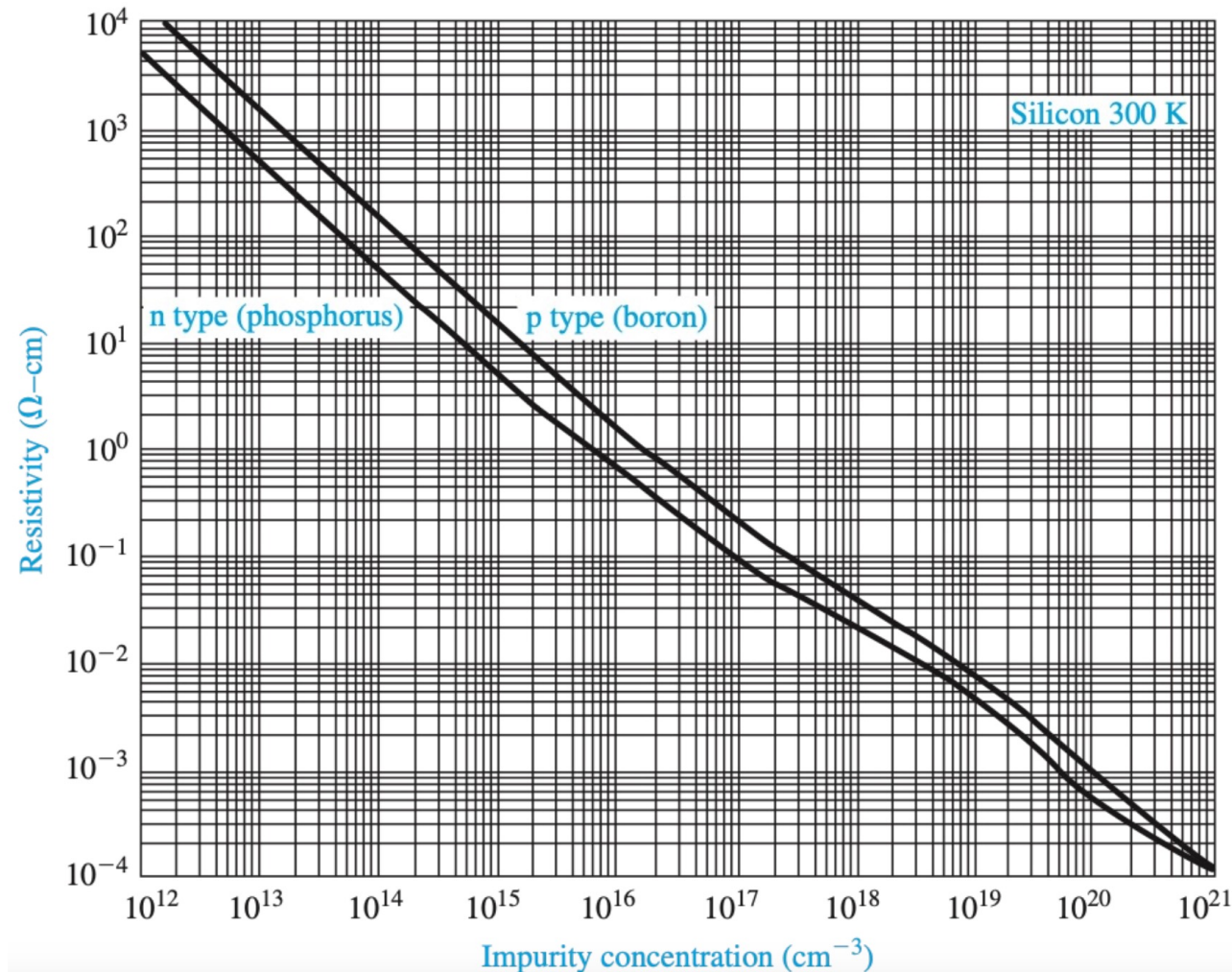

Resistivity, hence conductivity, changes over many orders of magnitudes; silicon is called **semiconductor**

Semiconductor basics (cont)



PERIODIC TABLE OF ELEMENTS


Discovered in 1871

Electron Configuration

<

Think Ångströms not nanometers

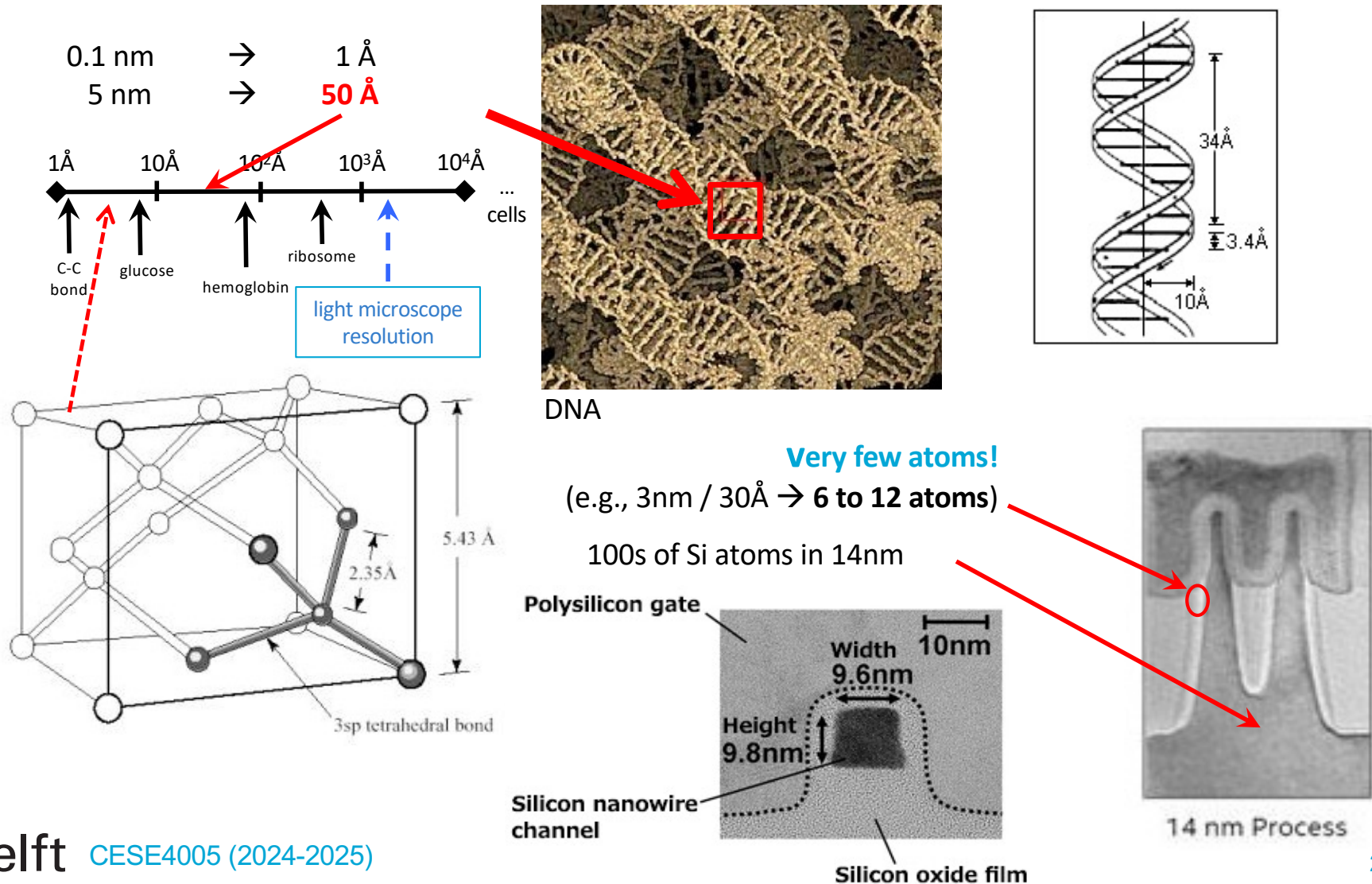We should steer the movements of almost each individual electron to solve our specific problem






Ongoing transistor device advancements



Qingzhu Zhang, Yongkui Zhang, Yanna Luo, Huaxiang Yin, *New structure transistors for advanced technology node CMOS ICs*, National Science Review, Volume 11, Issue 3, March 2024, nwae008, <https://doi.org/10.1093/nsr/nwae008>

The MOS FET transistor

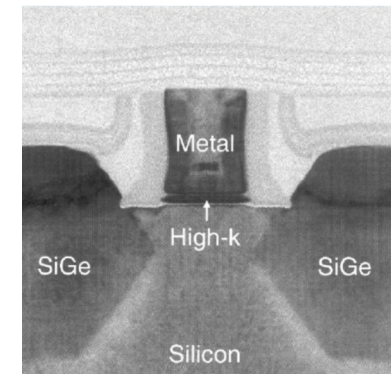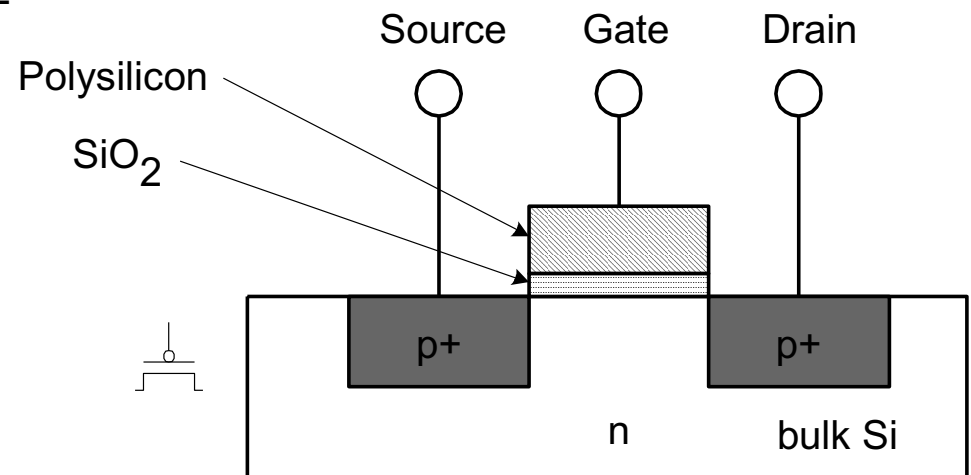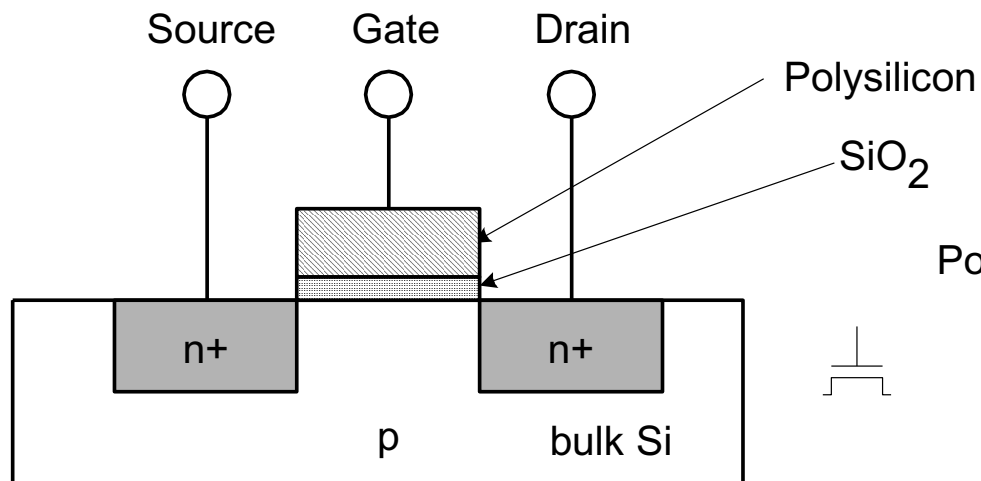- MOS FET (**M**etal-**O**xide **S**emiconductor **F**ield-**E**ffect **T**ransistor): a sandwich structure of p-type Si, n-type Si and insulator (SiO_2) materials
- It comes in two flavors: **nMOS** and **pMOS**:



Next Time

We continue ...